
 


 Question 1 (50 points total). Consider the following two circuit configurations. Both circuits are in fact identical except that the  $V_{DD}$  and GND terminals are swapped.  $R$  is a non-zero resistive load. Assume long channel devices and ignore channel length modulation.




Circuit A




Circuit B

 (a) (15 points) Sketch, not necessary to scale, the IV-curve for the transistor in circuit A. The x-axis is  $V_{DS}$ , and the y-axis is current  $I_D$ . Show also the IV-curve of the resistor in the plot to determine  $I_{D1}$ .



*Write in Exam Book Only*

 
(b) (15 points) Sketch, not necessary to scale, the IV-curve for the transistor in circuit B. The x-axis is  $V_{DS}$  and the y-axis is current  $I_D$ . Show also the IV-curve of the resistor in the plot to determine  $I_{D2}$ .



(c) (20 points) Which current,  $I_{D1}$  or  $I_{D2}$ , is larger? Justify your answer.

*Write in Exam Book Only*

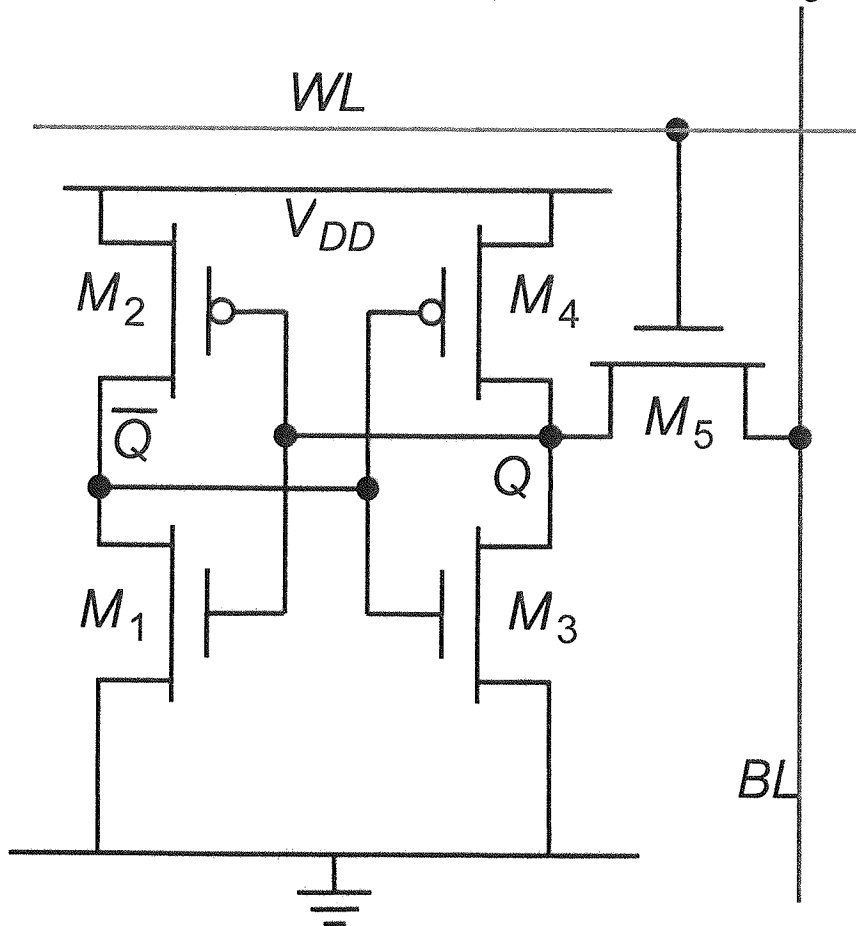Question 2. (50 points) Consider the following 5-Transistor SRAM cell design. Answer the following questions based on your understanding of ratioed logic. Use  $V_T$  as the threshold voltage (for NMOS and PMOS) and  $V_M$  as the switching threshold of inverters.



- (a) (15 points) Suppose  $V_Q$  is currently  $V_{DD}$ . Now, BL is pulled down to ground and WL is enabled. Discuss *qualitatively* the required sizing of the transistors to write 0 into Q (or making  $V_Q = 0V$ ). (You should identify the transistors forming the ratioed logic and state how the appropriate sizing of the ratioed logic could be determined, e.g., “transistors M1 and M5 form a ratioed logic and should be sized such that  $V_Q$  is less than  $V_{T,M3}$  when  $V_{WL}$  is high.” Do not attempt to solve equations.)
- (b) (15 points) Suppose  $V_Q$  is currently  $0V$ . Now, BL is pulled up to  $V_{DD}$  and WL is enabled. Discuss *qualitatively* the required sizing of transistors to write 1 into Q (or making  $V_Q = V_{DD}$ ).
- (c) (20 points) Assume that you have performed the appropriate sizing of transistors so that 0 and 1 can be written into Q correctly. Suppose WL is disabled and the voltage at node Q is either  $V_{DD}$  or  $0V$ . Suppose BL is now pre-charged to  $V_{DD}$  before we enable WL to perform a read operation. Is it possible to perform a read safely? In other words, can the transistors  $M_{1..5}$  work together to successfully pull BL to the voltage  $V_Q$ ? Justify your answer. If your answer is negative, propose a solution to overcome the problem without adding transistors.